

**Course Name:** System Design using Verilog

**Name:** D Nelson Eugene

**Roll No:** KVLSI2501121

**Date of Submission:** 31-05-2025 (Saturday)

Q1. Design a single State Transition Diagram (STD) for a Mealy-based sequence detector that detects overlapping occurrences of the following binary sequences:

a) 01011

b) 11001

c) 1100

Write down the Verilog code for the generated STD for the given sequences.

Soln: **RTL CODE**

```
module sequence_detector (
```

```
    input clk,
```

```
    input rst,
```

```
    input in,
```

```
    output reg out
```

```
);
```

```
    parameter S0 = 4'd0,
```

```
            S1 = 4'd1,
```

```
            S2 = 4'd2,
```

```
            S3 = 4'd3,
```

```
            S4 = 4'd4,
```

```
            S5 = 4'd5,
```

```

    S6 = 4'd6,

    S7 = 4'd7,

    S8 = 4'd8;

reg [3:0] current_state, next_state;

always @(*) begin

    next_state = current_state;

    out = 0;

    case (current_state)

        S0: begin

            if (in == 1) next_state = S5;

            else      next_state = S1;

        end

        S1: begin

            if (in == 1) next_state = S2;

            else      next_state = S1;

        end

        S2: begin

            if (in == 1) next_state = S5;

            else      next_state = S3;

        end

        S3: begin

            if (in == 1) next_state = S4;

            else      next_state = S1;

        end

        S4: begin

            if (in == 1) begin

                next_state = S0;

                out = 1; // 01011 detected
            end
        end
    endcase
end

```

```

    end else begin

        next_state = S3;

    end

end

S5: begin

    if (in == 1) next_state = S6;

    else      next_state = S1;

end

S6: begin

    if (in == 1) next_state = S6;

    else      next_state = S7;

end

S7: begin

    if (in == 1) next_state = S8;

    else begin

        next_state = S0;

        out = 1; // 1100 detected

    end

end

S8: begin

    if (in == 1) next_state = S6;

    else begin

        next_state = S0;

        out = 1; // 11001 detected

    end

end

end

default: begin

    next_state = S0;

```

```

        out = 0;

    end

endcase

end

// Sequential block: state register
always @(posedge clk or posedge rst) begin

    if (rst)

        current_state <= S0;

    else

        current_state <= next_state;

    end

endmodule

```

## Testbench

```

`timescale 1ns/1ps

module sequence_detector_tb;

    reg clk;

    reg rst;

    reg in;

    wire out;

    sequence_detector dut (

        .clk(clk),

        .rst(rst),

        .in(in),

        .out(out)

    );

```

```
always #5 clk = ~clk;
```

```
initial begin
```

```
    $dumpfile("sequence_detector.vcd");
```

```
    $dumpvars(0, sequence_detector_tb);
```

```
    clk = 0;
```

```
    rst = 1;
```

```
    in = 0;
```

```
    #10;
```

```
    rst = 0;
```

```
    $display("Time\tin\tout");
```

```
    // Sequence: 01011
```

```
    in = 0; #10;
```

```
    $display("%0t\t%b\t%b", $time, in, out);
```

```
    in = 1; #10;
```

```
    $display("%0t\t%b\t%b", $time, in, out);
```

```
    in = 0; #10;
```

```
    $display("%0t\t%b\t%b", $time, in, out);
```

```
    in = 1; #10;
```

```
    $display("%0t\t%b\t%b", $time, in, out);
```

```
    in = 1; #10; // Should produce out = 1
```

```
    $display("%0t\t%b\t%b", $time, in, out);
```

```
// Sequence: 1100
```

```
in = 1; #10;
```

```
$display("%0\t\t%b\t%b", $time, in, out);
```

```
in = 1; #10;
```

```
$display("%0\t\t%b\t%b", $time, in, out);
```

```
in = 0; #10;
```

```
$display("%0\t\t%b\t%b", $time, in, out);
```

```
in = 0; #10; // Should produce out = 1
```

```
$display("%0\t\t%b\t%b", $time, in, out);
```

```
// Sequence: 11001
```

```
in = 1; #10;
```

```
$display("%0\t\t%b\t%b", $time, in, out);
```

```
in = 1; #10;
```

```
$display("%0\t\t%b\t%b", $time, in, out);
```

```
in = 0; #10;
```

```
$display("%0\t\t%b\t%b", $time, in, out);
```

```
in = 0; #10;
```

```
$display("%0\t\t%b\t%b", $time, in, out);
```

```
in = 1; #10; // Should produce out = 1
```

```
$display("%0\t\t%b\t%b", $time, in, out);
```

```
$display("Test completed");
```


```
#20;
```

**\$finish;**


**end**

**endmodule**

**Waveform**

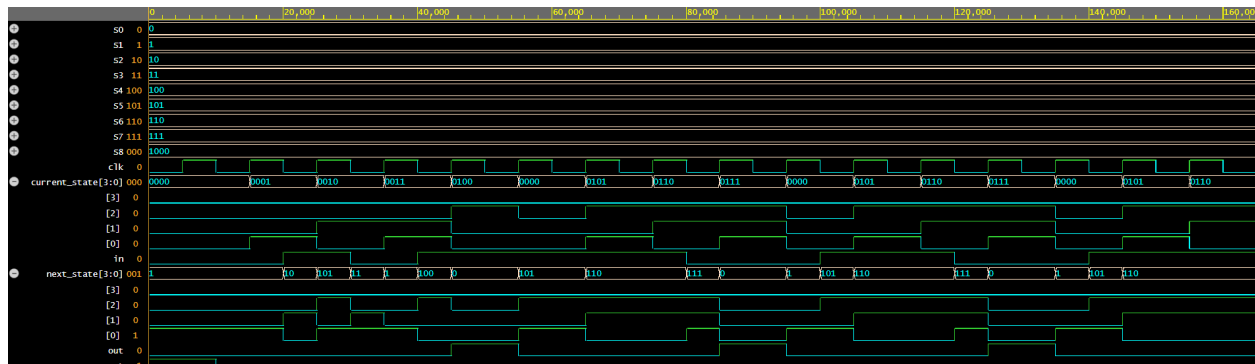

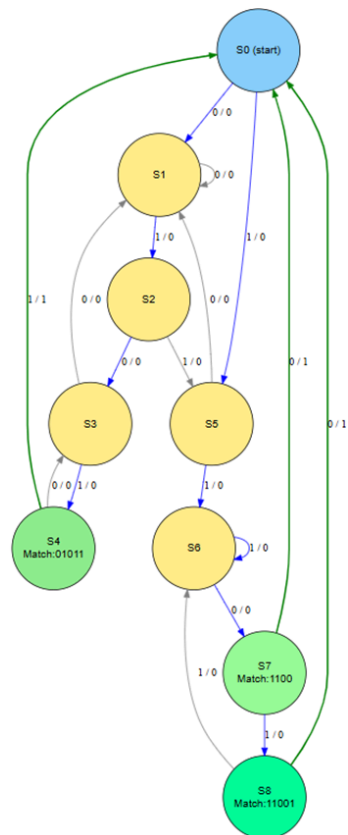**Final Mealy State diagram that detects all the input sequences**



**Q2.**Design a Verilog module for a Washing Machine with the following specifications:  
Functional Requirements: The machine has six states: a) IDLE: Waiting for user to start  
b) FILL: Filling water (2 minutes) c) WASH: Washing clothes (20 minutes) d) RINSE: Clothes Rinse (10 minutes) e) DRAIN: Draining water (3 minutes) f) SPIN: Spin clothes (5 minutes) After completing all these steps, a DONE/BEEP signal should be high for 30 seconds.

Soln: RTL Code

```
module washing_machine (
```

```
    input clk,
```

```
    input rst,
```

```
    input start,
```

```
    output reg fill,
```

```
    output reg wash,
```

```
    output reg rinse,
```

```
    output reg drain,
```

```
    output reg spin,
```

```
    output reg beep
```

```
);
```

```
// State encoding
```

```
parameter IDLE  = 3'd0;
```

```
parameter FILL  = 3'd1;
```

```
parameter WASH  = 3'd2;
```



```

parameter RINSE = 3'd3;

parameter DRAIN = 3'd4;

parameter SPIN = 3'd5;

parameter DONE = 3'd6;

reg [2:0] current_state, next_state;

reg [15:0] timer; // Enough to hold time in seconds

// State update logic

always @(posedge clk or posedge rst) begin

    if (rst) begin

        current_state <= IDLE;

        timer <= 0;

    end else begin

        current_state <= next_state;

        if (current_state != next_state)

            timer <= 0;

        else

            timer <= timer + 1;

    end

end

```

```
// Next state and output logic
```

```
always @(current_state or start or timer) begin
```

```
    // Default outputs
```

```
    fill = 0;
```

```
    wash = 0;
```

```
    rinse = 0;
```

```
    drain = 0;
```

```
    spin = 0;
```

```
    beep = 0;
```

```
    next_state = current_state;
```

```
    case (current_state)
```

```
        IDLE: begin
```

```
            if (start)
```

```
                next_state = FILL;
```

```
        end
```

```
        FILL: begin
```

```
            fill = 1;
```

```
            if (timer >= 120) // 2 minutes
```

```
                next_state = WASH;
```

```
        end
```

WASH: begin

wash = 1;

if (timer >= 1200) // 20 minutes

next\_state = RINSE;

end

RINSE: begin

rinse = 1;

if (timer >= 600) // 10 minutes

next\_state = DRAIN;

end

DRAIN: begin

drain = 1;

if (timer >= 180) // 3 minutes

next\_state = SPIN;

end

SPIN: begin

spin = 1;

if (timer >= 300) // 5 minutes

next\_state = DONE;

```
end

DONE: begin

    beep = 1;

    if (timer >= 30) // Beep for 30 seconds

        next_state = IDLE;

    end
```

```
endcase
```

```
end
```

```
endmodule
```

## Test bench

```
`timescale 1ns / 1ps
```

```
module washing_machine_tb;
```

```
    reg clk;
```

```
    reg rst;
```

```
    reg start;
```

```
    wire fill, wash, rinse, drain, spin, beep;
```

```
    washing_machine dut (
```

```
        .clk(clk),
```

```
        .rst(rst),
```

```
        .start(start),
```

```
.fill(fill),  
  
.wash(wash),  
  
.rinse(rinse),  
  
.drain(drain),  
  
.spin(spin),  
  
.beep(beep)  
  
);
```

```
// Clock generation: 1Hz clock => 1 cycle = 1 second (for simulation purpose,  
use faster clock in real sim)
```

```
always #5 clk = ~clk; // 10ns period = 100MHz clock
```

```
initial begin
```

```
    $dumpfile("washing_machine.vcd");
```

```
    $dumpvars(0, washing_machine_tb);
```

```
    clk = 0;
```

```
    rst = 1;
```

```
    start = 0;
```

```
    // Reset pulse
```

```
    #10;
```

```
    rst = 0;
```

```
    // Wait a bit then start machine
```

```
#10;
```

```
start = 1;
```

```
#10;
```

```
start = 0; // Pulse
```

```
// Simulate enough time to go through all states
```

```
// Total simulated time:
```

```
// FILL (120) + WASH (1200) + RINSE (600) + DRAIN (180) + SPIN (300) + DONE  
(30) = 2430 sec
```

```
// We reduce scale to make simulation fast: 1 simulated second = 10ns
```

```
#25000; // ~2.5k simulated seconds
```


```
$display("Simulation finished.");
```

```
$finish;
```


```
end
```

```
endmodule
```

## Waveform

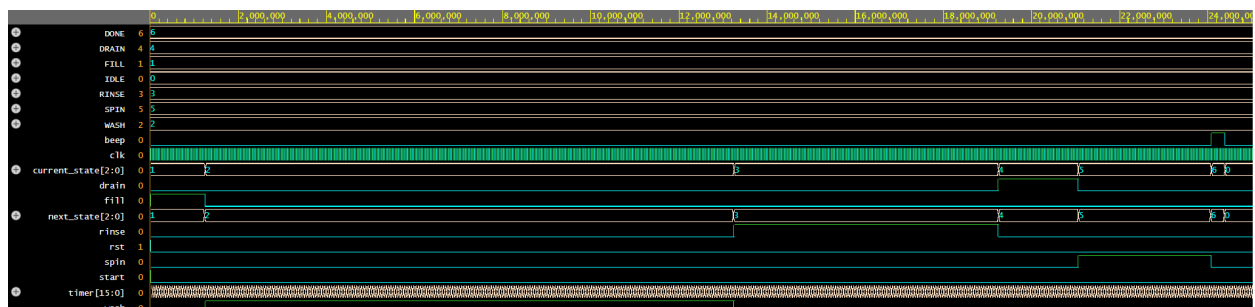

## State Diagram of its working

 

**Q3.Design and implement the I2C Bus Protocol using Verilog on Modelsim.**

**RTL Code and its Tb**

**// I2C Master Module**

**module i2c\_master (**

**input wire clk,**

**input wire reset,**

**input wire start,**

**input wire [6:0] slave\_addr,**

**input wire [7:0] data,**

**output reg sda,**

**output reg scl,**

**output reg done**

**);**

**// State encoding using parameter**

**parameter IDLE = 3'b000;**

**parameter START = 3'b001;**

**parameter ADDRESS = 3'b010;**

**parameter DATA = 3'b011;**

**parameter STOP = 3'b100;**



```
reg [2:0] current_state, next_state;
```

```
reg [3:0] bit_count; // to count up to 8 bits
```

```
// Clock divider to slow down SCL relative to clk might be needed in practice
```

```
// For simplicity, toggle scl every clk posedge for now
```

```
always @(posedge clk or posedge reset) begin
```

```
    if (reset) begin
```

```
        current_state <= IDLE;
```

```
        done <= 0;
```

```
        sda <= 1;
```

```
        scl <= 1;
```

```
        bit_count <= 0;
```

```
    end else begin
```

```
        current_state <= next_state;
```

```
    end
```

```
end
```

```
// Control sda, scl and state transitions
```

```
always @(posedge clk or posedge reset) begin
```

```
    if (reset) begin
```

```
        sda <= 1;
```

```
        scl <= 1;
```

```
bit_count <= 0;
```

```
done <= 0;
```

```
end else begin
```

```
case (current_state)
```

```
  IDLE: begin
```

```
    done <= 0;
```

```
    sda <= 1;
```

```
    scl <= 1;
```

```
    bit_count <= 0;
```

```
    if (start)
```

```
      next_state <= START;
```

```
    else
```

```
      next_state <= IDLE;
```

```
  end
```

```
  START: begin
```

```
    // Start condition: SDA goes low while SCL is high
```

```
    sda <= 0;
```

```
    scl <= 1;
```

```
    bit_count <= 0;
```

```
    next_state <= ADDRESS;
```

end

ADDRESS: begin

scl <= ~scl; // toggle clock

if (scl == 0) begin

// On low edge, set SDA with address bit

sda <= slave\_addr[6 - bit\_count];

end else begin

if (bit\_count == 6) begin

bit\_count <= 0;

next\_state <= DATA;

end else begin

bit\_count <= bit\_count + 1;

next\_state <= ADDRESS;

end

end

end

DATA: begin

scl <= ~scl; // toggle clock

if (scl == 0) begin

// On low edge, set SDA with data bit

```

        sda <= data[7 - bit_count];

    end else begin

        if (bit_count == 7) begin

            bit_count <= 0;

            next_state <= STOP;

        end else begin

            bit_count <= bit_count + 1;

            next_state <= DATA;

        end

    end

end

end

STOP: begin

    // Stop condition: SDA goes high while SCL is high

    scl <= 1;

    sda <= 0; // first maintain SDA low

    #1; // wait some time unit before releasing SDA

    sda <= 1;

    done <= 1;

    next_state <= IDLE;

end

```

```

        default: begin

            sda <= 1;

            scl <= 1;

            done <= 0;

            next_state <= IDLE;

        end

    endcase

end

end

endmodule

// I2C Slave Module

module i2c_slave (

    input wire clk,

    input wire reset,

    input wire sda,

    input wire scl,

    output reg [7:0] received_data,

    output reg data_ready

);

    reg [3:0] bit_count;

```

```
always @(posedge scl or posedge reset) begin
```

```
    if (reset) begin
```

```
        received_data <= 0;
```

```
        data_ready <= 0;
```

```
        bit_count <= 0;
```

```
    end else begin
```

```
        if (bit_count < 8) begin
```

```
            received_data[7 - bit_count] <= sda; // Receive data
```

```
            bit_count <= bit_count + 1;
```

```
            data_ready <= 0;
```

```
        end else begin
```

```
            data_ready <= 1; // Data received
```

```
            bit_count <= 0;
```

```
        end
```

```
    end
```

```
end
```

```
endmodule
```

```
// Testbench: tb_i2c
```

```
module tb_i2c;
```

```
    reg clk;
```

```
reg reset;

reg start;

reg [6:0] slave_addr;

reg [7:0] data;

wire sda;

wire scl;

wire done;

wire [7:0] received_data;

wire data_ready;

i2c_master master (

    .clk(clk),

    .reset(reset),

    .start(start),

    .slave_addr(slave_addr),

    .data(data),

    .sda(sda),

    .scl(scl),

    .done(done)

);

i2c_slave slave (
```

```

        .clk(clk),

        .reset(reset),

        .sda(sda),

        .scl(scl),

        .received_data(received_data),

        .data_ready(data_ready)
    );

initial begin

    clk = 0;

    reset = 1;

    start = 0;

    slave_addr = 7'b1010101;

    data = 8'b11001100;

    #20 reset = 0;

    #20 start = 1;

    #10 start = 0;

    #500; // enough time for transfer

    $stop;

end

always #5 clk = ~clk; // 100MHz clock

```



**initial begin**

```
$monitor("%t | sda=%b scl=%b done=%b received_data=%b data_ready=%b",  
$time, sda, scl, done, received_data, data_ready);
```

**end**

**endmodule**

## Simulation Output

```
#          0 | sda=1 scl=1 done=0 received_data=00000000 data_ready=0  
#         65 | sda=0 scl=1 done=0 received_data=00000000 data_ready=0  
#        75 | sda=1 scl=1 done=0 received_data=00000000 data_ready=0  
#        85 | sda=1 scl=0 done=0 received_data=00000000 data_ready=0  
#        95 | sda=1 scl=1 done=0 received_data=10000000 data_ready=0  
#       105 | sda=1 scl=0 done=0 received_data=10000000 data_ready=0  
#       115 | sda=1 scl=1 done=0 received_data=11000000 data_ready=0  
#       125 | sda=1 scl=0 done=0 received_data=11000000 data_ready=0  
#       135 | sda=1 scl=1 done=0 received_data=11100000 data_ready=0  
#       145 | sda=1 scl=0 done=0 received_data=11100000 data_ready=0  
#       155 | sda=1 scl=1 done=0 received_data=11110000 data_ready=0  
#       165 | sda=1 scl=0 done=0 received_data=11110000 data_ready=0  
#       175 | sda=1 scl=1 done=0 received_data=11111000 data_ready=0  
#       185 | sda=1 scl=0 done=0 received_data=11111000 data_ready=0  
#       195 | sda=1 scl=1 done=0 received_data=11111100 data_ready=0  
#       205 | sda=1 scl=0 done=0 received_data=11111100 data_ready=0  
#       215 | sda=1 scl=1 done=0 received_data=11111110 data_ready=0  
#       225 | sda=1 scl=0 done=0 received_data=11111110 data_ready=0
```

```
#      235 | sda=1 scl=1 done=0 received_data=11111111 data_ready=0
#      245 | sda=1 scl=0 done=0 received_data=11111111 data_ready=0
#      255 | sda=1 scl=1 done=0 received_data=11111111 data_ready=1
#      265 | sda=1 scl=0 done=0 received_data=11111111 data_ready=1
#      275 | sda=1 scl=1 done=0 received_data=11111111 data_ready=0
#      285 | sda=1 scl=0 done=0 received_data=11111111 data_ready=0
#      295 | sda=1 scl=1 done=0 received_data=11111111 data_ready=0
#      305 | sda=1 scl=0 done=0 received_data=11111111 data_ready=0
#      315 | sda=1 scl=1 done=0 received_data=11111111 data_ready=0
#      325 | sda=1 scl=0 done=0 received_data=11111111 data_ready=0
#      335 | sda=1 scl=1 done=0 received_data=11111111 data_ready=0
#      345 | sda=1 scl=0 done=0 received_data=11111111 data_ready=0
#      355 | sda=1 scl=1 done=0 received_data=11111111 data_ready=0
#      365 | sda=1 scl=0 done=0 received_data=11111111 data_ready=0
#      375 | sda=1 scl=1 done=0 received_data=11111111 data_ready=0
#      385 | sda=1 scl=0 done=0 received_data=11111111 data_ready=0
#      395 | sda=1 scl=1 done=0 received_data=11111111 data_ready=0
#      405 | sda=1 scl=0 done=0 received_data=11111111 data_ready=0
#      415 | sda=1 scl=1 done=0 received_data=11111111 data_ready=0
#      425 | sda=1 scl=0 done=0 received_data=11111111 data_ready=0
#      435 | sda=1 scl=1 done=0 received_data=11111111 data_ready=1
#      445 | sda=1 scl=0 done=0 received_data=11111111 data_ready=1
#      455 | sda=1 scl=1 done=0 received_data=11111111 data_ready=0
#      465 | sda=1 scl=0 done=0 received_data=11111111 data_ready=0
#      475 | sda=1 scl=1 done=0 received_data=11111111 data_ready=0
```

```

#      485 | sda=1 scl=0 done=0 received_data=11111111 data_ready=0

#      495 | sda=1 scl=1 done=0 received_data=11111111 data_ready=0

#      505 | sda=1 scl=0 done=0 received_data=11111111 data_ready=0

#      515 | sda=1 scl=1 done=0 received_data=11111111 data_ready=0

#      525 | sda=1 scl=0 done=0 received_data=11111111 data_ready=0


#      535 | sda=1 scl=1 done=0 received_data=11111111 data_ready=0

#      545 | sda=1 scl=0 done=0 received_data=11111111 data_ready=0

# ** Note: $stop   : D:/Xilinx/work/i2c_bus.v(186)

```

## Waveform

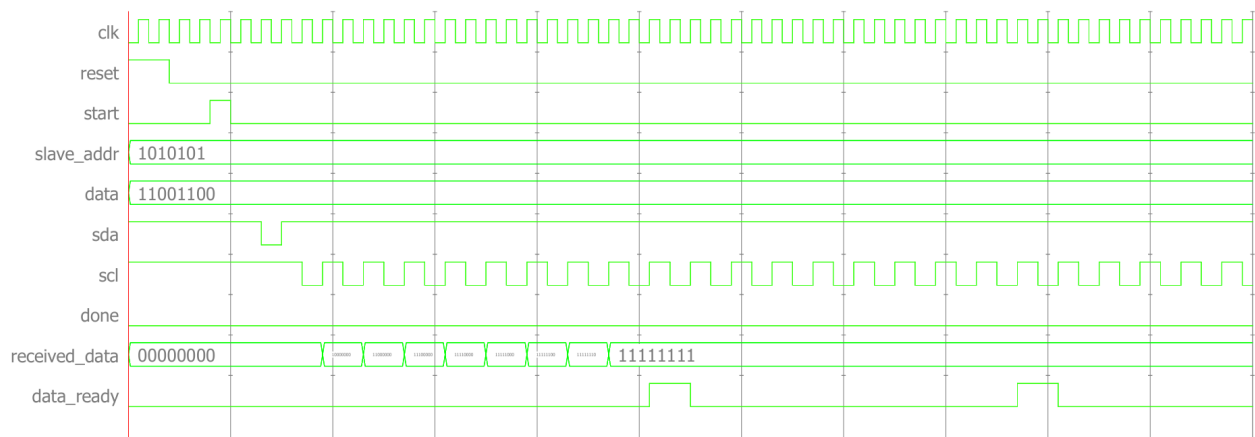

## FSM BLOCK OF I2C BUS

